

---

# Lecture 15:

## Datapath Functional Units

# Overview

---

## Reading

W&E 8.2.8 Shifters

W&E 8.2.7 Multiplication

## Introduction

This lecture continues to discuss how to build functions that are used in datapaths. It begins by talking about shifters, and then briefly describes multiplication. After describing these two functions, we take a step back, and look at how datapaths are put together, and how the control for the datapath is generated.

# Shifters

---

There are many different kinds of shifters.

- Simple Shifter


Shift the number to the right or left and fill-in with zeros

- Arithmetic Shifter

Left shifts are the same as simple shifter, but on right shifts use the sign bit to fill-in the new blank spaces (-2 shifted right by 1 gives -1)<sup>1</sup>

- Barrel Shifter

 Wrap the number onto a circle. The shift amount indicates where the new MSB will be. (Useful for rotating the bytes in a 32-bit word)




---

1. Need to be careful about arithmetic right shifts. '1' right shifted by 1 is 0. '-1' right shifted by 1 is -1

 
# Funnel Shifter

Is the most general kind of shifter

- Can do all the other shifts.
- Concatenates two n-bit words together and then selects any contiguous n-bit subfield.



 - If A=B get a barrel shifter
- If A = sign bit, get arithmetic shifts
- And it does byte inserts too.
- Can implement this shifter using a cross-bar switch, where the inputs are vertical and the output are horizontal



# Shifter Design

Can think of a shifter as a large fanin multiplexer

- Connect the correct input to the output


For a completely general Funnel Shifter there are  $2n$  inputs

This is 64 inputs for a 32 bit machine

- Clearly, we don't want full CMOS transmission gates


Reduce the number of control lines by using nMOS only gates

 Use precharging - the input will selectively discharge the output.


 
# Shifter Layout



It is a little tricky, but is not very bad:



Inputs are driven from both sides, and then run diagonally through the array. Control runs vertically, and the output runs horizontally.
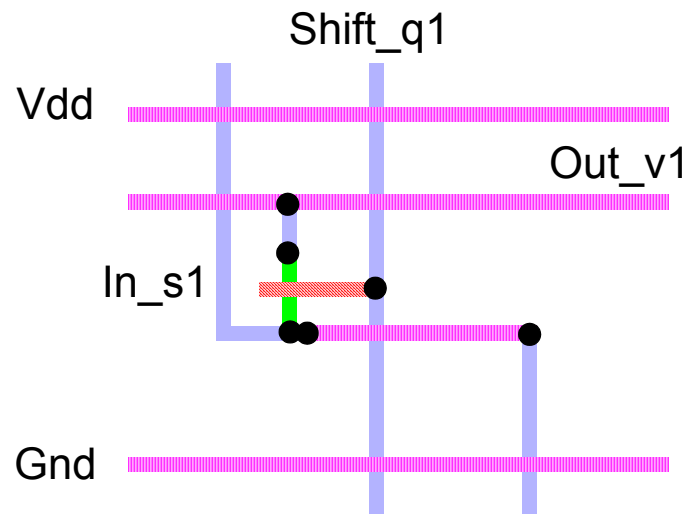 
# Bitslice Shifter Works Well

Even though there are many wires that flow between bits, this data is regular and can easily be embedded in the cell. In our system we do not have diagonal wires, so we make them stair steps




Cells don't use Vdd, Gnd, but need to route them for the other cells. The shift cells should not be mirrored (all nMOS so there is no need), but can fit in with a mirrored datapath (just change Vdd Gnd names)

# Shifter Layout

---

Diagonal dataflow mapped into a regular manhattan layout.

 Using M2 data, M1 control. (cell is rotated so data flows vertically)





# Multiplication

---

In binary it is pretty simple.

- The bit multiplication is just an AND gate
- All you need to do is add up the partial products

<b>multiplicand:</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>12</b>			
<b>multiplier:</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>5</b>			
	<hr/>							
	<b>1</b>	<b>1</b>	<b>0</b>	<b>0</b>				
	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>4 partial products</b>			
	<b>1</b>	<b>1</b>	<b>0</b>	<b>0</b>				
	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>				
	<hr/>							
	<b>0</b>	<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>60</b>

**repeat n times:**

**compute partial product; shift; add**

# Multiplier Implementation

---

Two approaches


- Shift and Add
- Parallel Multipliers

Shift and Add

- Use a standard adder, and multiple cycles to add up all the partial products.
- Use the LSB of the multiplier to decide whether to add the multiplicand this cycle
- Then shift both the multiplier and the partial result right by one, and repeat.

# Serial Multiplier

---

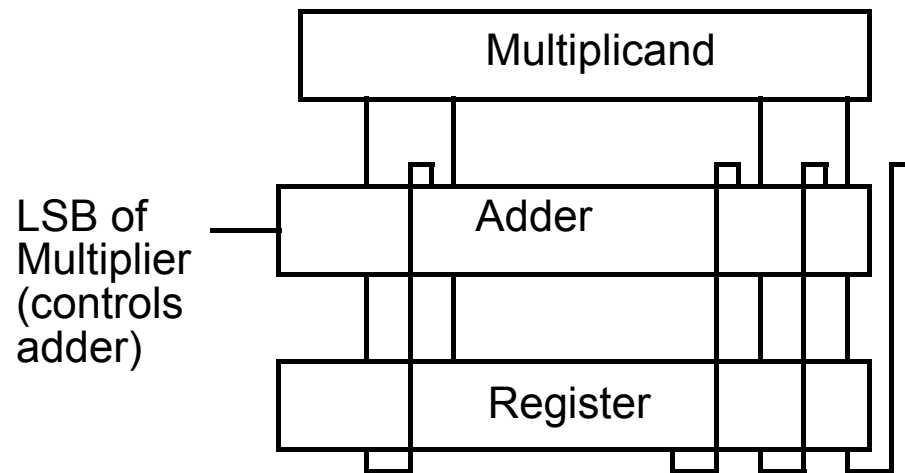


This hardware generates a  $2n$  bit result, so you need to catch the bits that shift off the end of the register. If you only wanted to generate an  $n$  bit result, then it would be better to shift the multiplicand to the left.<sup>1</sup>

---

1. There are many techniques to make this faster. One is to have some hardware find the '1's in the multiplier since, the zeros don't do much. For this we need to shift the result by the number of zeros skipped plus one. There is also a way to recode the multiplier (Booth Coding) to reduce the number of steps, but it is outside the scope of this class.

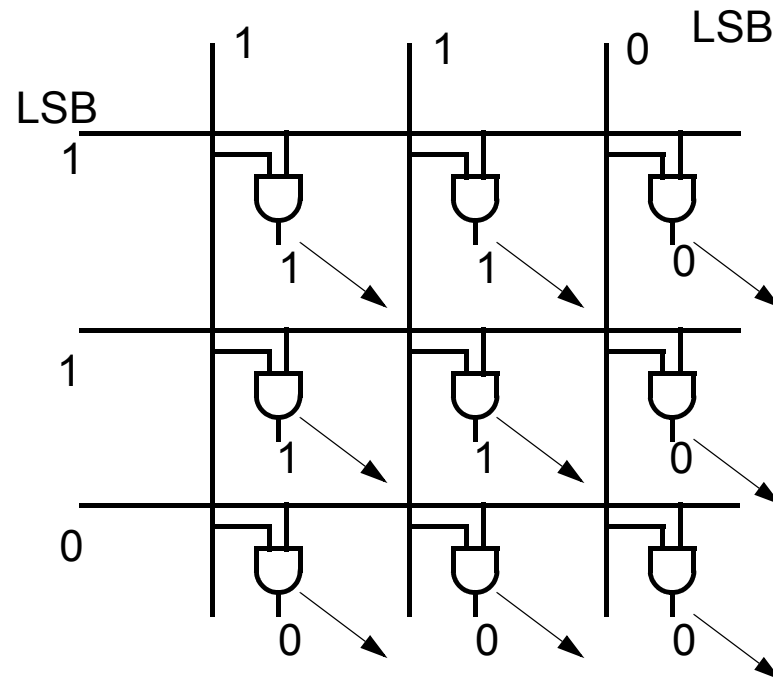
# Parallel Multipliers

Idea is to generate all the partial products in parallel, and then add them together by using lots of adders, rather than lots of cycles:


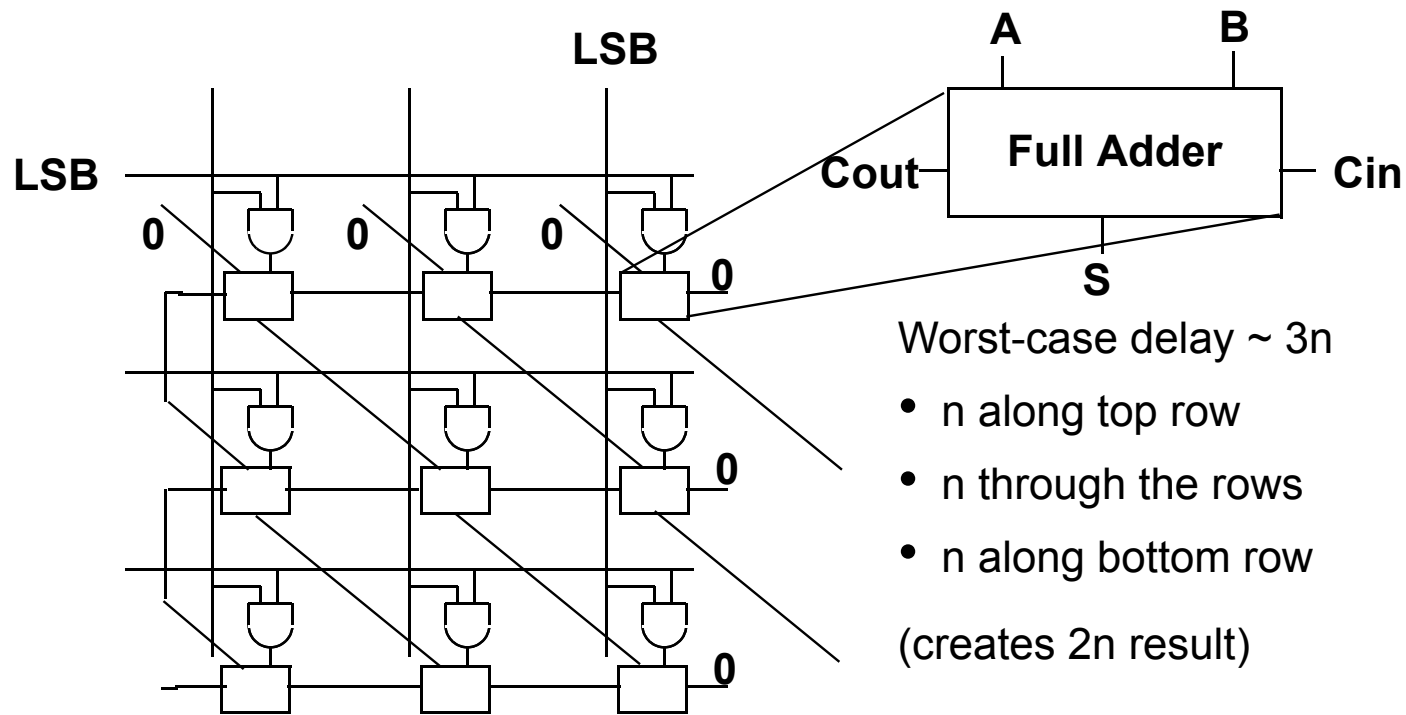
# Adding the Partial Products

- Use a ripple adder in each row (carry ripple right to left)
- Sums ripple diagonally (down and to the right)



## A Better Way

---

There are a number of better ways to do parallel multiplication.

- Look at a full adder again


Takes three inputs of equal weight, and adds them together

Produces two outputs of different weights


So a row of FAs could add three partial products and produce two outputs (one is shifted by one)

Next row could add one more partial product

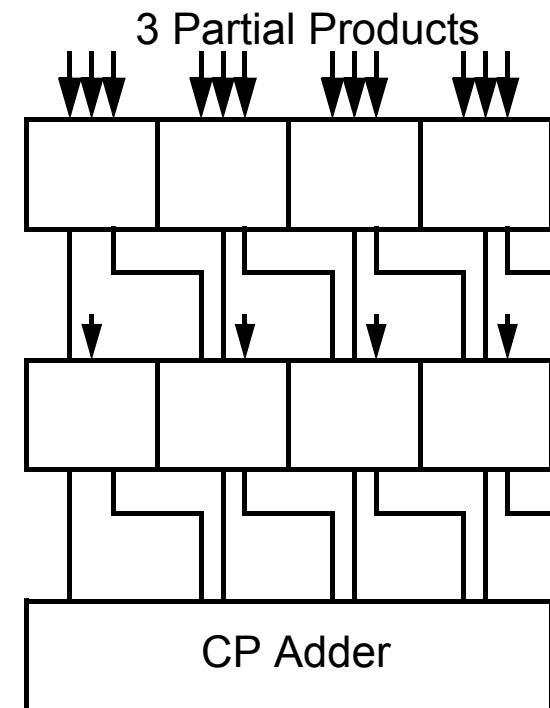Need Carry Propagate Adder at the end to reduce the final two partial products into a single sum. This can be a simple ripple adder, or a more complex Carry Look Ahead Adder for better performance.




# Carry Save Adder Array

 
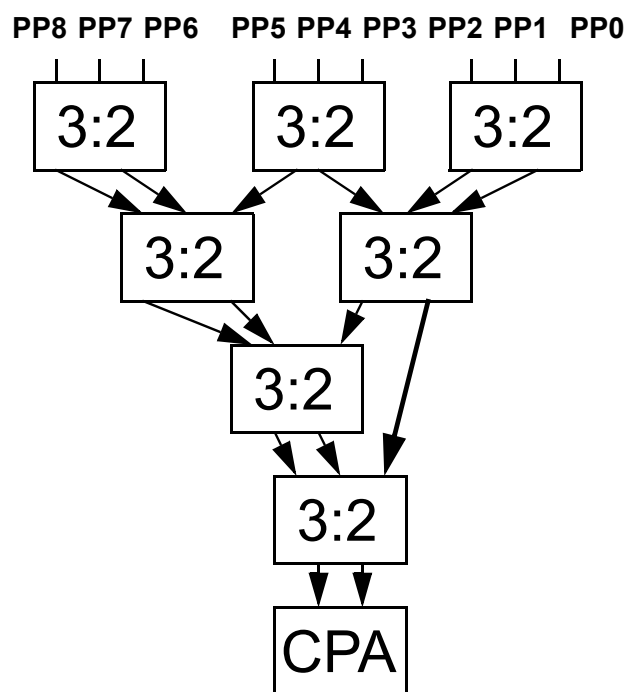
## + Multiplier Trees

---


Can reduce the number of series carry-save adders, by adding more of the partial products in parallel. Use a tree of adders. First proposed by Wallace (Wallace Trees)




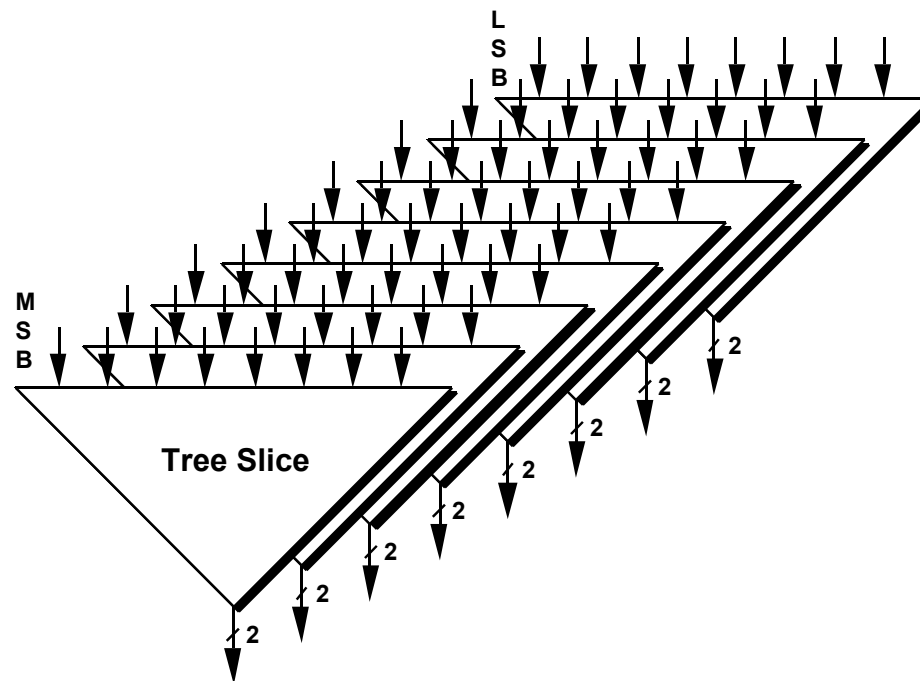
## + Multiplier Tree Slices

An  $n \times n$  bit multiplier requires  $2n$  slices to produce the complete product. Some bits from one slice must go to the adjacent slice further complicating the wiring.



## + Multiplier Trees

---

- Multiplier trees are pretty fast.
- Time is proportional to the  $\text{Log}(n)$
- Can pipeline the levels in the tree to increase the data rate

BUT

- Takes a lot of hardware
- Wiring is a mess

While you draw a tree, the adders must be layed out in a linear array (Each adder is  $n$ -bits wide already).


This means that there are number of wiring tracks that need to allocated to each bit slice.

And unlike arrays, some wires in a tree are not very short.

Use only when you need the speed (or have a program to layout the tree).

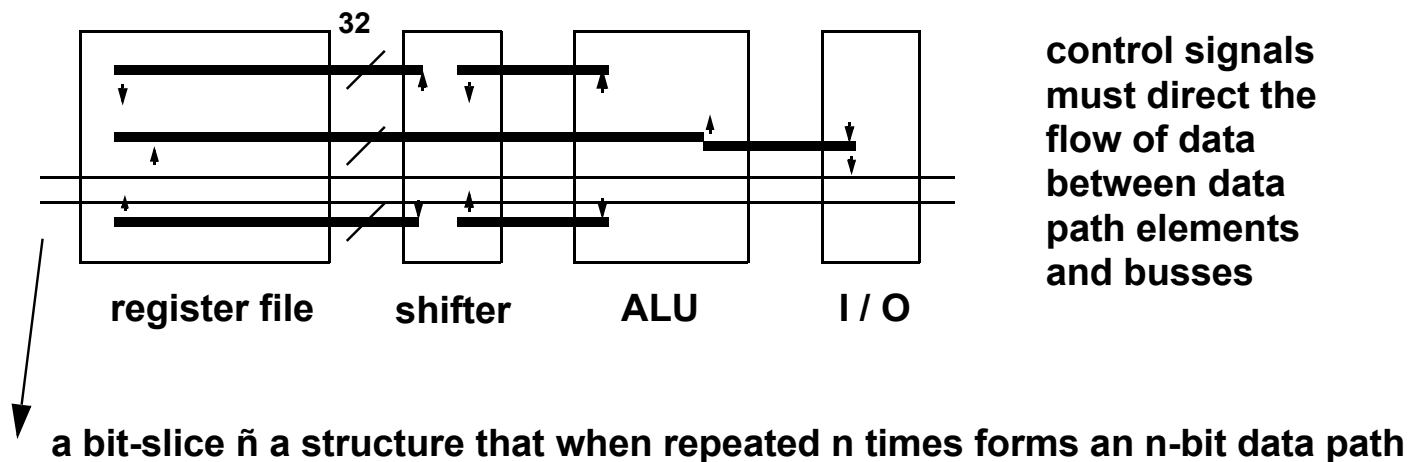
# Datapath Summary

- Composed of register files, latches, ALUs, latches, Shifter, latches, other functional units, latches
- Uses a bitsliced layout organization. Wordslices often pipelined.
- Uses a bused based communication protocol
- Wiring in the datapath is regular.




- Problem is that all cells must have the same height -- means you need to estimate which cell is the tallest, and use that to set bit pitch.

# Bit Slice Design

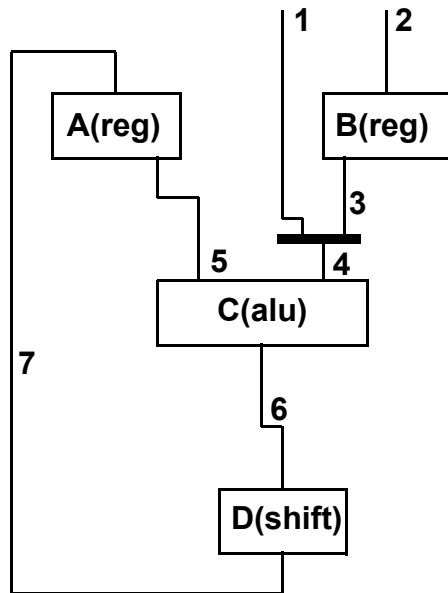

 if all busses are 32 bits  
this is a nightmare to  
interconnect (note: ALU  
inputs need to be  
interleaved)




leave room for  
busses even in  
cells that don't  
need them
 
# Datapath Control

---


So far we have talked about what goes into the datapath. These function units / latches / muxes manipulate the data itself. But this logic is only part of the whole chip. Something needs to tell the datapath elements what to do. And this is the function of the control.



When the datapath is pipelined (multiple parts of operations in progress simultaneously), the control keeps track of the status of all of the pieces.

# Control

---

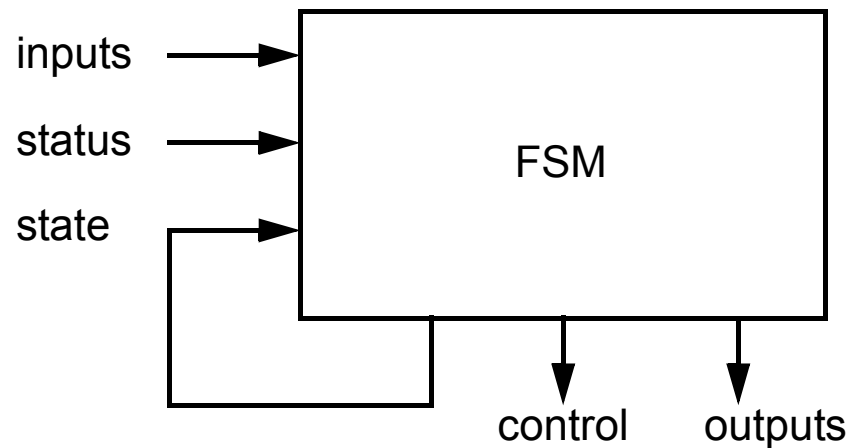

It is usually an FSM since some operations that the chip performs take multiple clock cycles, and the controller must know where it is in the instruction.

In pipelined microprocessors, each instruction may take  $n$  cycles to complete, but the next instructions are started before previous ones have finished. The controller must track which instruction is at each function in each cycle. Complexity explodes with pipeline depth.

# Control Implementation

---

In an ideal world:

- Write HDL (Verilog) of the control
  - Define the inputs / outputs / states of the controller
- Use synthesis tools to convert it into logic
- Use place and routing tools to convert logic into layout

But the world is never so ideal:

- The automated-tool-only approach is both too big and too slow
- Need to help the tools along

# Real Controller Design Flow

---

1. Write a description of the controller in Verilog

Simulate it to get it to work

Think up hard cases to try to break it

2. Use synthesis tools to generate the logic

Look at the critical paths

If (where) they are too slow,

Try to figure out why the tool generated the logic it did

Change the section in the Verilog that generated the slow logic

Goto 1.

3. Use standard cell place and route system to generate the layout

Look at area, make sure aspect ratio is ok, and total area is ok

Look at speed. If slow, try to change the placement. If that doesn't work then change the Verilog and goto 1.



# Local Control


---

Don't want to generate all the control signals in the controller.

- Too many wires needed between sections
- Poor control of datapath timing

Use a pitch-matched local control section aligned on top of datapath

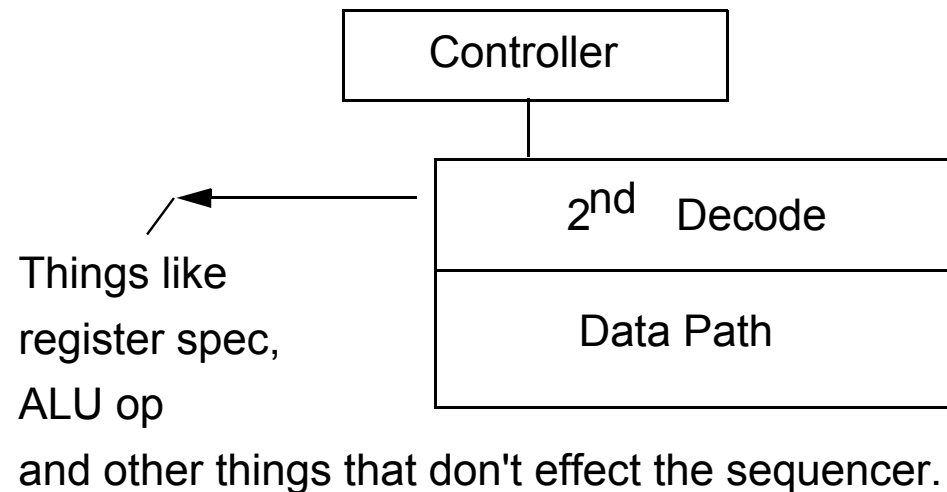- Generate true/complement pairs, buffered-up versions, and clock-qualification here.



# Local Control

---

Run a track on top of the datapath for control drivers for the data path.

- Create true and complement control when needed.
- Do buffering and clock qualification (when needed)

On top of this track place local decoders to reduce # of control wires.

